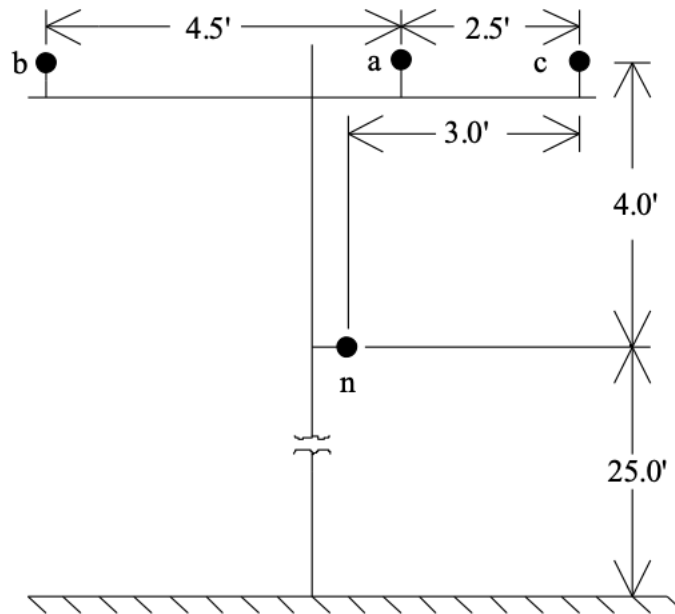


ECE 1710 – Power Distribution and Smart Grids
Approximate Methods

1. Determine the positive sequence impedance for the following transmission line



The phase conductors are 397, 500 cmil, 26/7 ACSR conductors and the neutral is a 4/0, 6/1 ACSR conductor.

Using MATLAB

```
phase_cond.r = 0.3;  
phase_cond.GMR = 0.0818;
```

```
zpos = transposedLineImpedance(phase_cond,f)
```

$$z_{pos} = 0.3 + j0.75 \, \Omega/mi$$

2. Repeat problem 1 using all aluminum conductor instead of ACSR. Comment on the difference. Also, comment on why one conductor would be selected over the other
3. A 2400 V lateral has the following loads

$$S_1 = 20 \, kW + j10 \, kvar$$

$$S_2 = 10 \text{ kW} + j8 \text{ kvar}$$

$$S_3 = 12 \text{ kW} + j7 \text{ kvar}$$

$$S_4 = 18 \text{ kW} + j7 \text{ kvar}$$

$$S_5 = 10 \text{ kW} + j12 \text{ kvar}$$

$$S_6 = 20 \text{ kW} + j15 \text{ kvar}$$

$$S_7 = 20 \text{ kW} + j12 \text{ kvar}$$

$$S_8 = 10 \text{ kW} + j10 \text{ kvar}$$

Using the the positive sequence per-phase impedance determined in problem 1, the line lengths between loads are

$$L_{12} = 1000 \text{ ft.}$$

$$L_{23} = 800 \text{ ft.}$$

$$L_{34} = 1000 \text{ ft.}$$

$$L_{45} = 1200 \text{ ft.}$$

$$L_{56} = 500 \text{ ft.}$$

$$L_{67} = 1500 \text{ ft.}$$

- a. Using a linear ladder network please calculate the voltage at each node, the current supplied to the network, and the Vdrop percent from source to load 7.
- b. Repeat this using the nonlinear iterative power flow solution.